

Weighted Moving Average Filter Documentation

Submitted by: Amr Hossam
GitHub Repo: https://github.com/amrhossam9/ADI_Assignments

Assignment Overview

implementing a **Weighted Moving Average Filter** using Verilog.

Key Specifications

$H(Z) = [1, 0.5, 0.25, 0.125]$

- Frequency:** 100 MHz
- Implementation:** Verilog
- Deliverables:**
 - Filter RTL
 - Filter Testbench

Filter RTL Design

Module: **Filter**

The **Filter** module takes an 8-bit input signal and applies a weighted moving average over the last three samples. The weightings used are powers of two to simplify the design, achieved using bit shifts.

Inputs:

- x:** 8-bit input signal
- CLK:** Clock signal
- RST:** Reset signal (active low)


Outputs:

- y:** 8-bit filtered output

Internal Registers:

- registers[0:2]:** Stores the last three input samples.

Wave form

 

Transcript

```
# input = 14
# Test      1 succeeded 14
# input = 65
# Test      2 succeeded 6f
# input = 27
# Test      3 succeeded 5e
# input = 43
# Test      4 succeeded 71
# input = 15
# Test      5 succeeded 4b
# input = 4d
# Test      6 succeeded 6b
# input = 21
# Test      7 succeeded 54
# input = 53
# Test      8 succeeded 78
# input = 58
# Test      9 succeeded 92
# input = 5f
# Test     10 succeeded a3
# input = 39
# Test     11 succeeded 88
# input = 0a
# Test     12 succeeded 48
# input = 1d
# Test     13 succeeded 3b
# input = 74
# Test     14 succeeded 8b
# input = 13
# Test     15 succeeded 55
# input = 69
# Test     16 succeeded 92
# input = 44
# Test     17 succeeded 8a
```

Verilog Code:

```
module Filter (  
    input wire [7:0] x,  
    input wire CLK, RST,  
    output reg [7:0] y  
);  
  
    reg [7:0] registers [2:0];  
    wire [7:0] val0, val1, val2;  
  
    assign val0 = registers[0] >> 1;  
    assign val1 = registers[1] >> 2;  
    assign val2 = registers[2] >> 3;  
  
    always @(posedge CLK or negedge RST)  
    begin  
        if(!RST)  
        begin  
            registers[0] <= 0;  
            registers[1] <= 0;  
            registers[2] <= 0;  
            y <= 0;  
        end  
        else  
        begin  
            y <= (x + val0 + val1 + val2);  
            registers[2] <= registers[1];  
            registers[1] <= registers[0];  
            registers[0] <= x;  
        end  
    end  
endmodule
```

Testbench for Filter

Testbench Code:

```
module Filter_TB ();

    reg [7:0] x_TB;
    reg CLK_TB, RST_TB;
    wire [7:0] y_TB;

    parameter CLK_PERIOD = 10;
    parameter N = 100;
    parameter DATA_LENGTH = 8;
    integer operations;

    reg [DATA_LENGTH - 1:0] Test_Inputs [N - 1:0];
    reg [DATA_LENGTH - 1:0] Expec_Outs [N - 1:0];

    initial begin
        $dumpfile("Filter_DUMP.vcd") ;
        $dumpvars;

        $readmemh("input.txt", Test_Inputs);
        $readmemh("output.txt", Expec_Outs);

        initialize();

        for (operations = 0; operations < N; operations = operations + 1)
            begin
                do_operation(Test_Inputs[operations], operations);
                checkout(Expec_Outs[operations], operations);
            end

        #100;
        $finish;
    end

    task initialize;
    begin
        CLK_TB = 0;
        x_TB = 0;
        rest();
    end
endtask

task rest;
begin
    RST_TB = 'b1;
    #CLK_PERIOD;
    RST_TB = 'b0;
    #CLK_PERIOD;
    RST_TB = 'b1;
```

```
end
endtask

task do_operation;
input reg [DATA_LENGTH - 1:0] INPUT_TEST;
input integer operation_number;
begin
    x_TB = INPUT_TEST;
    #CLK_PERIOD;

    $display("input = %h", INPUT_TEST);
end
endtask

task checkout;
input reg [DATA_LENGTH - 1:0] expected_output;
input integer operation_number;
reg [DATA_LENGTH - 1:0] general_output;
begin
    general_output = y_TB;

    if (expected_output == general_output)
    begin
        $display("Test %d succeded %h", operation_number + 1, general_output);
    end
    else
    begin
        $display("Test %d failed %h", operation_number + 1, general_output);
    end
end
endtask

always #(CLK_PERIOD/2) CLK_TB = ~CLK_TB;

Filter DUT(
    .x(x_TB),
    .CLK(CLK_TB),
    .RST(RST_TB),
    .y(y_TB)
);

endmodule
```