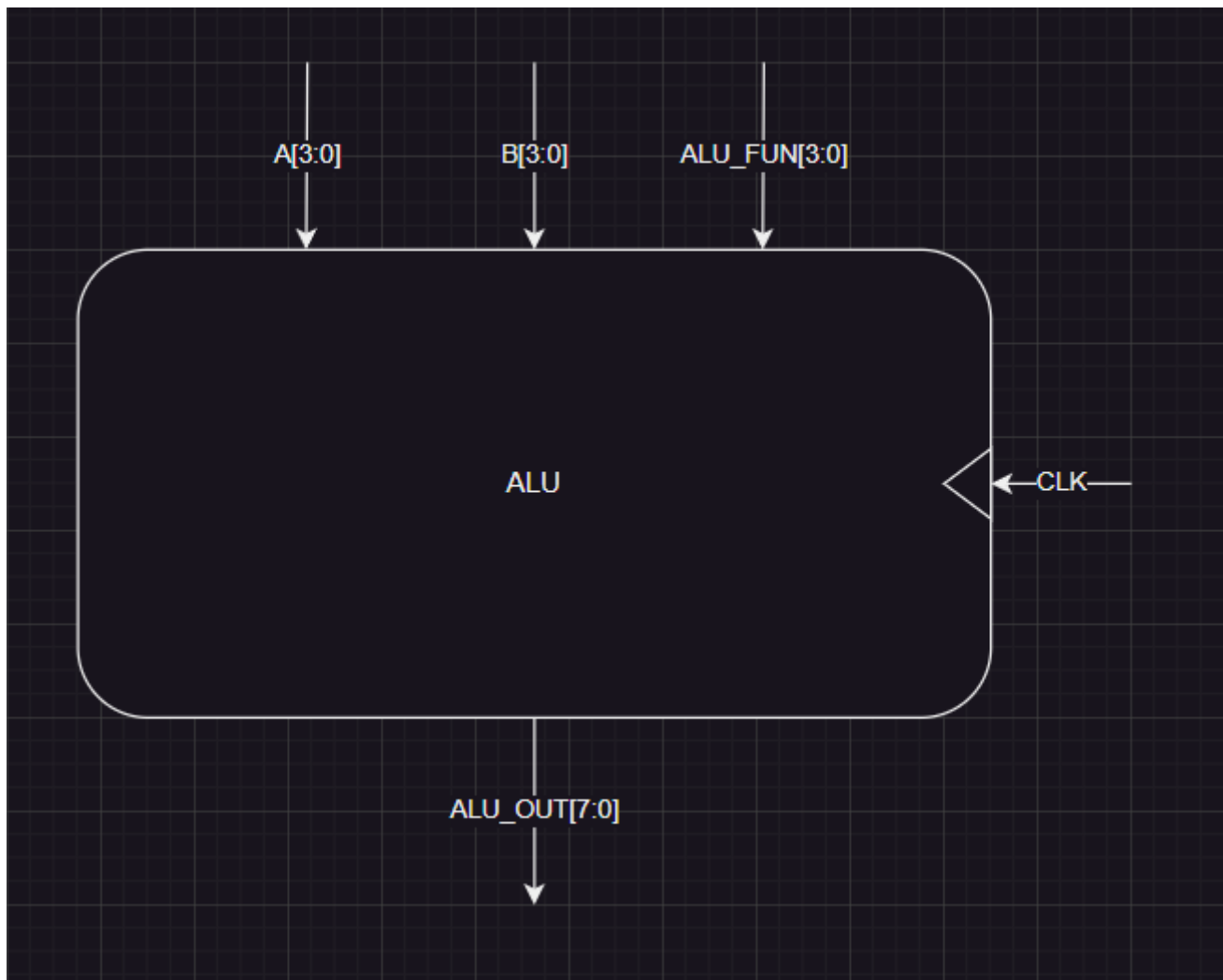


Verification Plan for ALU



- **Inputs:**

- **A** (4-bit input)
- **B** (4-bit input)
- **ALU_FUN** (2-bit control signal)
- **CLK** (clock)

- **Output:**

- **ALU_OUT** (8-bit result of ALU operation)

- **ALU Operations:**

- **ALU_FUN** = 2'b00: Addition ($\text{ALU_OUT} = A + B$)
- **ALU_FUN** = 2'b01: Subtraction ($\text{ALU_OUT} = A - B$)
- **ALU_FUN** = 2'b10: Multiplication ($\text{ALU_OUT} = A * B$)
- **ALU_FUN** = 2'b11: Division ($\text{ALU_OUT} = A / B$)

Test Scenarios

- **Addition:** Test multiple combinations of **A** and **B** with $ALU_FUN = 2'b00$.
 - Case 1: $A = 4'b0001, B = 4'b0010$ ($1 + 2 = 3$)
 - Case 2: $A = 4'b1111, B = 4'b0001$ ($15 + 1 = 16$)
 - **Subtraction:** Test multiple combinations of **A** and **B** with $ALU_FUN = 2'b01$.
 - Case 1: $A = 4'b0100, B = 4'b0011$ ($4 - 3 = 1$)
 - Case 2: $A = 4'b0001, B = 4'b0100$ ($1 - 4 = -3$)
 - **Multiplication:** Test multiple combinations of **A** and **B** with $ALU_FUN = 2'b10$.
 - Case 1: $A = 4'b0010, B = 4'b0011$ ($2 * 3 = 6$)
 - Case 2: $A = 4'b1111, B = 4'b0010$ ($15 * 2 = 30$)
 - **Division:** Test multiple combinations of **A** and **B** with $ALU_FUN = 2'b11$.
 - Case 1: $A = 4'b0100, B = 4'b0010$ ($4 / 2 = 2$)
 - Case 2: $A = 4'b1111, B = 4'b0001$ ($15 / 1 = 15$)
 - **Maximum Values:** Check operations with the largest values of **A** and **B** (e.g., $A = 4'b1111, B = 4'b1111$).
 - **Zero Values:** Test with **A** or **B** being **0** to check behavior during operations like addition, subtraction, multiplication, and division.
-